

LM2841 Evaluation Board

National Semiconductor
Application Note 1876
Clinton Jensen
April 6, 2009



Introduction

The LM2841 is a PWM DC/DC buck (step-down) regulator. With a wide input range from 4.5V-42V, it is suitable for a wide range of applications from automotive to power conditioning from unregulated sources. The LM2841 evaluation board is designed to provide the design engineer with a fully functional power converter based on the buck topology to evaluate the LM2841 series of buck regulators. The evaluation board comes populated with the LM2841YMK-ADJL but can easily be modified to accommodate any of the LM2841 regulator ICs.

Features

- 4.5V to 42V Input Voltage Range
- 3.3V Output Voltage
- Up to 300 mA Output Current
- 89% Efficiency at 300 mA
- Switching Frequency of 1.25 MHz
- Frequency Foldback Current Limit of 550 mA
- Internal Compensation

Shutdown Operation

The evaluation board includes a 3 pin header and a jumper to select whether the device is on or off. Placing the jumper in the "ON" position ties $\overline{\text{SHDN}}$ to VIN and enables the device. Placing the jumper in the "OFF" position ties $\overline{\text{SHDN}}$ to GND and disables the device. The jumper may be removed and a logic signal may be applied to the center pin to test startup and shutdown of the device.

Adjusting the Output Voltage

The output voltage can be changed from 3.3V to another voltage by adjusting the feedback resistors using the following equation:

$$V_{\text{OUT}} = V_{\text{FB}}(1 + (R1/R2))$$

Where V_{FB} is 0.76V.

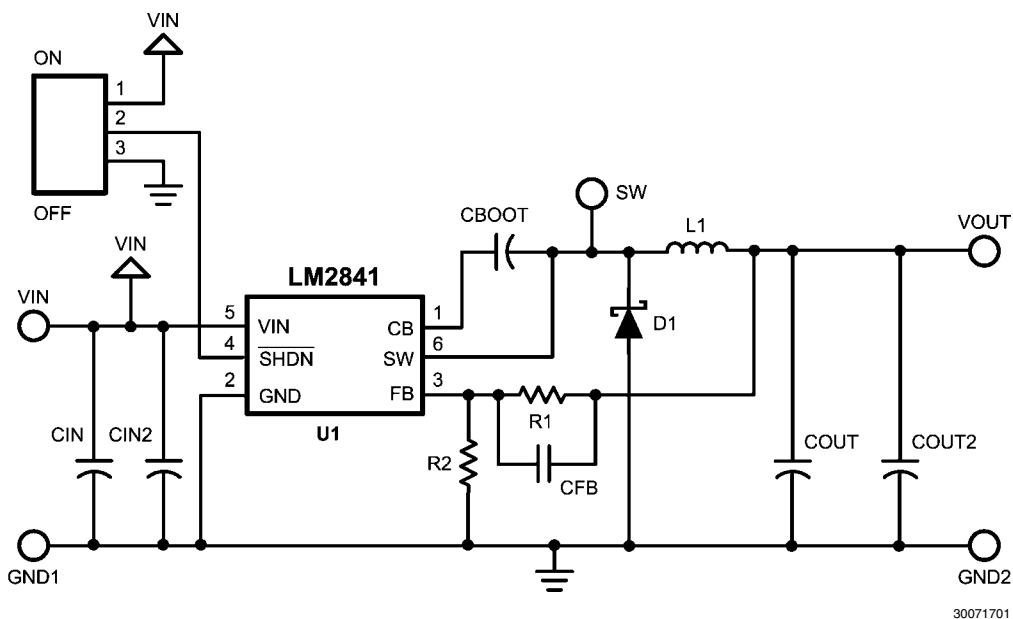



FIGURE 1. LM2841 Evaluation Board Schematic

Bill of Materials (BOM)

ID	Part Number	Type	Size	Parameters	Qty	Vendor
U1	LM2841YMK-ADJL	Buck Regulator	TSOT-6		1	NSC
L1	DO1608C-153MLC	Inductor	1608	15 μ H, 0.9A	1	Coilcraft
D1	MA2YD2600L	Diode	SOD-123	60V, 800 mA	1	Panasonic
CIN	GRM31CR71H225KA88	Capacitor	1206	2.2 μ F, 50V	1	Murata
CIN2	OPEN					
COUT	GRM32ER60J476ME20	Capacitor	1210	47 μ F, 6.3V	1	Murata
COUT2	OPEN					
CFB	OPEN					
CBOOT	VJ0805Y154KXXA	Capacitor	0805	0.15 μ F	1	Vishay/ Vitraron
R1	CRCW08053K40FKEA	Resistor	0805	3.4 k Ω	1	Vishay
R2	CRCW08051K02FKEA	Resistor	0805	1.02 k Ω	1	Vishay
ON/OFF		1X3 header	HDR1X3	0.100 Spacing	1	
ON/OFF*	382811-6	Shunt			1	Tyco/Amp
VIN, VOUT, GND1, GND2, SW	1502-2	Test Post	TP 1502		5	Keystone


Typical Performance Characteristics

Efficiency vs. Load Current

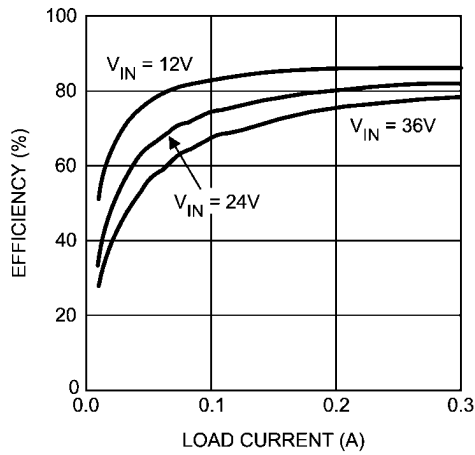

30071705

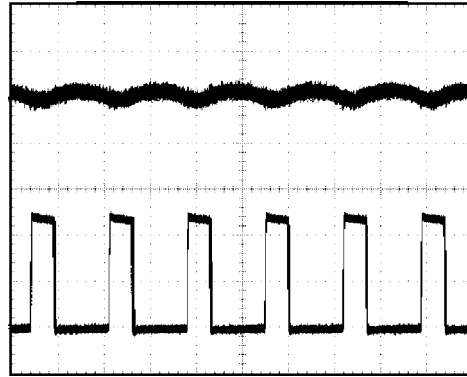
Switching Node and Output Voltage Waveforms



30071724

$V_{IN} = 12V$, $V_{OUT} = 3.3V$, $I_{OUT} = 200\text{ mA}$
 Top trace: VOUT, 10 mV/div, AC Coupled
 Bottom trace: SW, 5V/div, DC Coupled
 T = 200 ns/div


Load Transient Waveforms

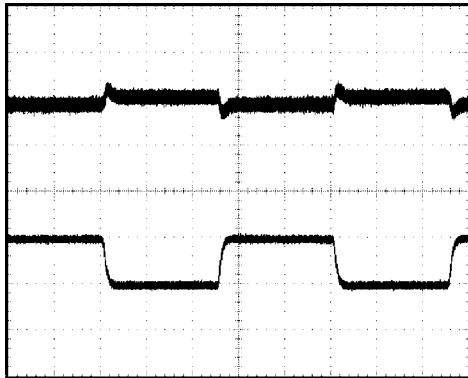

30071725

$V_{IN} = 12V$, $V_{OUT} = 3.3V$, $I_{OUT} = 300\text{ mA to } 200\text{ mA to } 300\text{ mA}$
 Top trace: VOUT, 20 mV/div, AC Coupled
 Bottom trace: IOUT, 100 mA/div, DC Coupled
 T = 200 $\mu\text{s/div}$


Startup Waveform

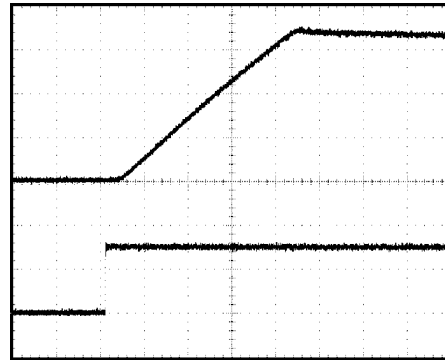

30071726


$V_{IN} = 12V$, $V_{OUT} = 3.3V$, $I_{OUT} = 50\text{ mA}$
 Top trace: VOUT, 1V/div, DC Coupled
 Bottom trace: SHDN, 2V/div, DC Coupled
 T = 40 $\mu\text{s/div}$

Layout

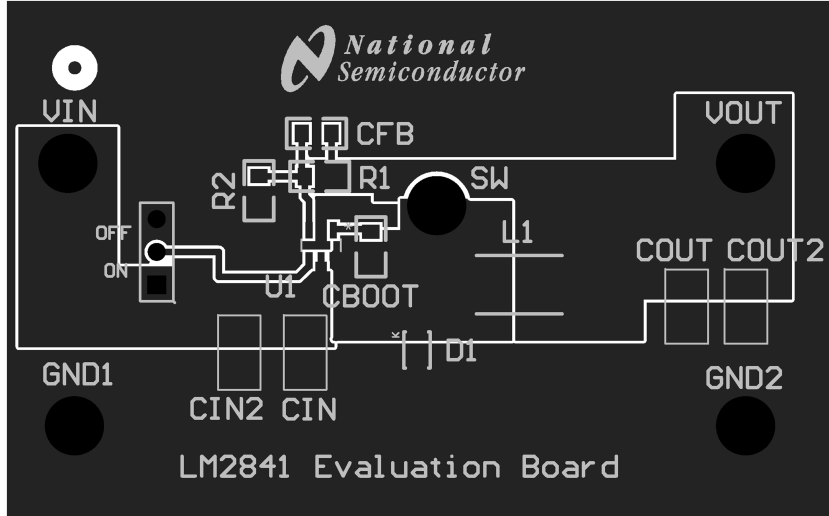

Top Layer and Top Overlay

30071720

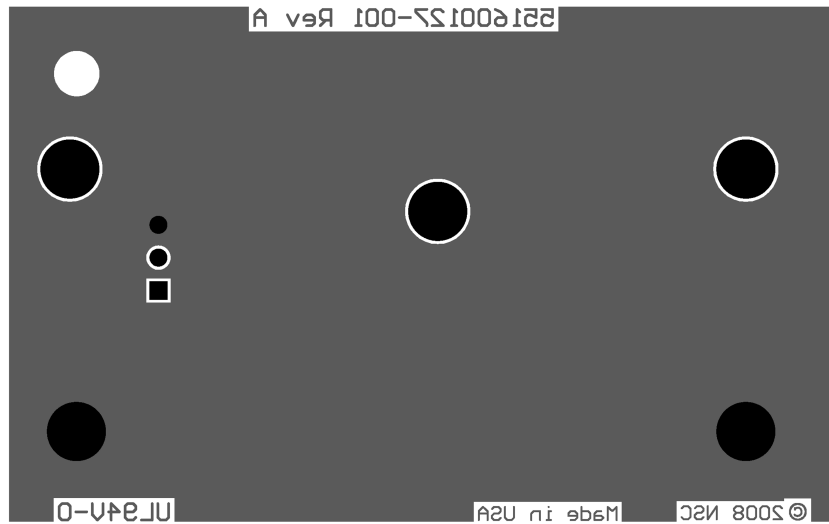

Bottom Layer and Bottom Overlay

30071723

Notes

AN-1876

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH® Tools	www.national.com/webench
Audio	www.national.com/audio	App Notes	www.national.com/appnotes
Clock and Timing	www.national.com/timing	Reference Designs	www.national.com/refdesigns
Data Converters	www.national.com/adc	Samples	www.national.com/samples
Interface	www.national.com/interface	Eval Boards	www.national.com/evalboards
LVDS	www.national.com/lvds	Packaging	www.national.com/packaging
Power Management	www.national.com/power	Green Compliance	www.national.com/quality/green
Switching Regulators	www.national.com/switchers	Distributors	www.national.com/contacts
LDOs	www.national.com/ldo	Quality and Reliability	www.national.com/quality
LED Lighting	www.national.com/led	Feedback/Support	www.national.com/feedback
Voltage Reference	www.national.com/vref	Design Made Easy	www.national.com/easy
PowerWise® Solutions	www.national.com/powerwise	Solutions	www.national.com/solutions
Serial Digital Interface (SDI)	www.national.com/sdi	Mil/Aero	www.national.com/milaero
Temperature Sensors	www.national.com/tempsensors	SolarMagic™	www.national.com/solarmagic
Wireless (PLL/VCO)	www.national.com/wireless	Analog University®	www.national.com/AU

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2009 National Semiconductor Corporation

For the most current product information visit us at www.national.com



National Semiconductor
Americas Technical
Support Center
Email: support@nsc.com
Tel: 1-800-272-9959

National Semiconductor Europe
Technical Support Center
Email: europe.support@nsc.com

National Semiconductor Asia
Pacific Technical Support Center
Email: ap.support@nsc.com

National Semiconductor Japan
Technical Support Center
Email: jpn.feedback@nsc.com